Shahjalal University of Science & Technology
Dept. of Electrical & Electronic Engineering
Course No: EEE 0713 3239
Power Electronics

Assessment #6

Total points: 10

Question: Derive the expression for the line-to-line RMS output voltage of a three-phase inverter operating in 120° conduction mode.