Shahjalal University of Science & Technology
Dept. of Electrical & Electronic Engineering
Course No: EEE 0713 3239
Power Electronics

Assessment #7

Total points: 10

Question: A single-phase full wave AC voltage controller has resistive load R = 10 ohm and the input voltage of V_s = 120V (rms), 60 Hz. The delay angles of thyristors T1 and T2 are 80 and 180+100 respectively. Draw the output waveform and Determine a) the rms output voltage V_o, b) the input power factor